

FAMU- FSU College of Engineering
Department of Electrical and Computer Engineering Spring
2024 Semester
EEL3705L Digital Logic Lab Report

Section No: 0002

Lab Instructor: Bruce Harvey

Lab No: Lab Project

Lab Title: Digital Combination Lock

Name: Ruth Massock

Partner's Name: Christopher Balthazar

Date Performed: 4/24/2024

Date Delivered: 4/25/2024

Contents

1 Introduction.....	3
2 Requirements	3
3 Theoretical Design	3
a) Design Narrative	3
b) Top-level design.....	4
c) Functional description of components	5
4 Synthesized Design	5
5 Simulation Results	8
6 Experimental Results	9
7 Summary	12
8 Lessons Learned.....	12

1 Introduction

In this lab project, we were assigned to design and implement a digital combination lock using the DE1-SoC board. Module locks are fundamental components in digital systems used for security and access control. They require users to input a specific sequence or password to gain access to a system or module. In this experiment, we implemented a module lock using Verilog HDL, targeting an FPGA or ASIC platform. The module lock design comprised state machines and combinational logic to validate the password input and control the lock's behavior accordingly. Our password was 11-17-46.

2 Requirements


This lab required some of the following to make this digital combinational lock. The lock should have the following states: STATE_s0, STATE_s1, STATE_s2, STATE_s3, STATE_unlock, and STATE_invalid. The lab had the following input ports: Clk: Clock input. Reset: Reset signal to initialize or reset the lock. pass1: 4-bit input for the first part of the password. pass2: 4-bit input for the second part of the password. The lab had the following output ports: out: Output signal indicating whether the lock is unlocked (1) or locked (0). hex0, hex1, hex2, hex3, hex4, hex5: Seven-segment display outputs to visualize the lock status.

3 Theoretical Design

Design Narrative


Our Verilog HDL module lock employs state machine logic and password verification for secure access control. It transitions between six states, unlocking upon correct password input. Synchronous logic ensures accurate transitions, while seven-segment displays offer visual feedback. Validation through simulation ensures reliable operation under diverse conditions, making our design a dependable solution for digital access control.


state diagram

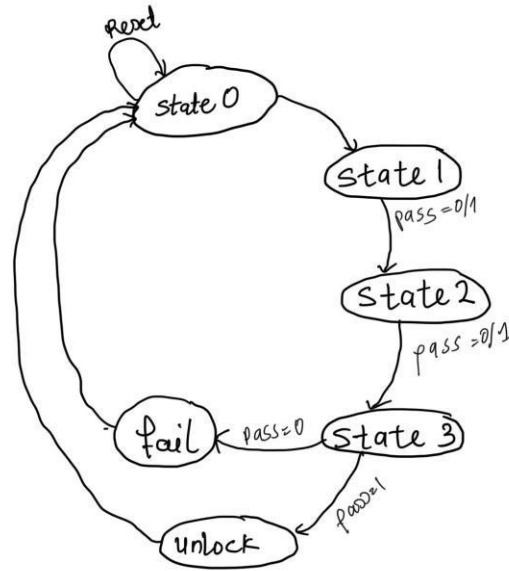


Top-level design

Top level design

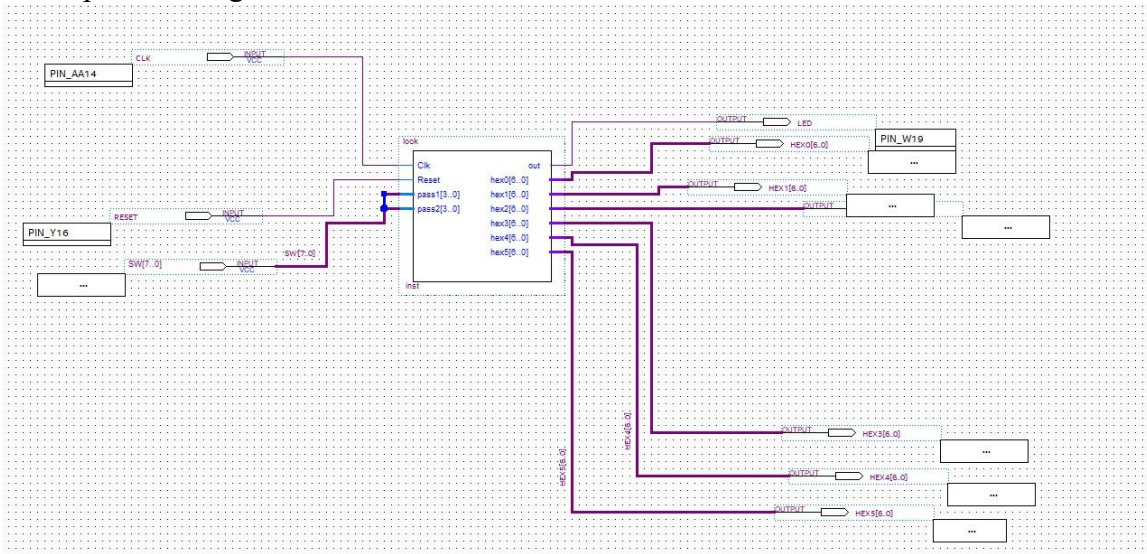

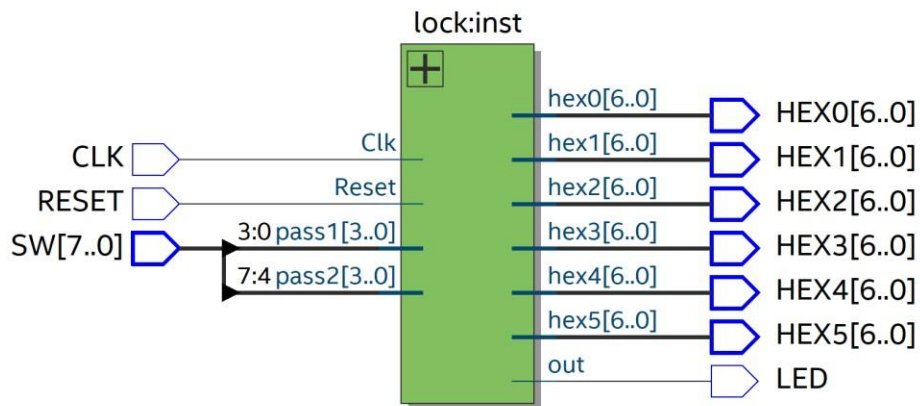

Hardware setup

 

Functional description of components

LED5 on the DE1 Soc Board serves as output to show lock is unlocked by lighting up (extra credit). Hex5 to Hex0 display entered password, unlock results of ||||| and failed results of -----. Switches from SW7 to SW0 are used to enter a pair of password number, key0 serves as a clock and key3 serves as the reset button

4 Synthesized Design

Verilog code for Combinational lock

```
1 //Names: Christopher Balthazar and Ruth Massock
2 //Semester: Spring 2024
3 //Lab Section:section 0002 Friday at 9pm
4 //Date Created: 04/24/2024
5 //Description: this code is lock that displays
6 //||||| for unlock ----- for failed and shows numbers been entered
7 module lock (
8     input wire clk,
9     input wire Reset,
10    input wire [3:0] pass1,
11    input wire [3:0] pass2,
12    output reg out,
13    output reg [6:0] hex0,    // Seven-segment display outputs
14    output reg [6:0] hex1,
15    output reg [6:0] hex2,
16    output reg [6:0] hex3,
17    output reg [6:0] hex4,
18    output reg [6:0] hex5
19 );
20
21 // Define states
22 localparam STATE_s0=3'b000,
23 STATE_s1=3'b001,
24 STATE_s2=3'b010,
25 STATE_s3=3'b011,
26 STATE_unlock = 3'b100,
27 STATE_invalid = 3'b101;
28
29 // Define state registers
30 reg [2:0] CurrentState,NextState;
31
32 // Define password array
33 reg [3:0] password [0:5];
34
35 // Seven-segment display outputs
36 reg [6:0] z;
37 reg [6:0] zz;
38
39 // Initialize password array: 11-17-46
40 initial begin
41     password[0] = 4'b0001; //1
42     password[1] = 4'b0001; //1
43     password[2] = 4'b0001; //1
44     password[3] = 4'b0111; //7
45     password[4] = 4'b0100; //4
46     password[5] = 4'b0110; //6
47 end
48
```

```

49 // State transition logic
50 always @(posedge clk) begin
51     if (Reset)
52         CurrentState <= STATE_s0;
53
54     else
55         CurrentState <= NextState;
56 end
57 always @(*) begin
58
59     NextState=CurrentState;
60     case (CurrentState)
61     STATE_s0: begin
62         NextState = STATE_s1;
63     end
64     STATE_s1: begin
65         if(pass1 == password[0] && pass2 == password[1])
66             NextState = STATE_s2;
67     end
68     STATE_s2: begin
69         if(pass1 == password[2] && pass2 == password[3])
70             NextState = STATE_s3;
71     end
72     STATE_s3: begin
73         if (pass1 == password[4] && pass2 == password[5])
74             NextState = STATE_unlock;
75     else
76         NextState = STATE_invalid;
77     end
78     STATE_unlock: begin
79         if (pass1 == 4'b0000 && pass2 == 4'b0000)
80             NextState = STATE_s0;
81         else
82             NextState = STATE_invalid;
83     end
84     STATE_invalid: begin
85         if (pass1 == 4'b0000 && pass2 == 4'b0000)
86             NextState = STATE_s0;
87         else
88             NextState = STATE_invalid;
89     end
90 endcase
91 end
92
93 // Output logic
94 always @(*) begin
95     out=0;
96     case (CurrentState)
97
98     STATE_s1: begin

```

```

97 STATE_s1: begin
98   out = 0;
99   // Define outputs for STATE_s1
100   hex5 = ~z;
101   hex4 = ~zz;
102 end
103 STATE_s2: begin
104   out = 0;
105   // Define outputs for STATE_s2
106   hex3 = ~z;
107   hex2 = ~zz;
108 end
109 STATE_s3: begin
110   out = 0;
111   // Define outputs for STATE_s3
112   hex1 = ~z;
113   hex0 = ~zz;
114 end
115 STATE_unlock: begin
116   out = 1;
117   // Define outputs for STATE_unlock
118   hex0 = 7'b1111001;
119   hex1 = 7'b1111001;
120   hex2 = 7'b1111001;
121   hex3 = 7'b1111001;
122   hex4 = 7'b1111001;
123   hex5 = 7'b1111001;
124 end
125 STATE_invalid: begin
126   out = 0;
127   // Define outputs for STATE_invalid
128
129   hex0 = 7'b0111111;
130   hex1 = 7'b0111111;
131   hex2 = 7'b0111111;
132   hex3 = 7'b0111111;
133   hex4 = 7'b0111111;
134   hex5 = 7'b0111111;
135 end
136 default: begin
137   out = 0;
138   hex0 = 7'b1111111; //blank display
139   hex1 = 7'b1111111;
140   hex2 = 7'b1111111;
141   hex3 = 7'b1111111;
142   hex4 = 7'b1111111;
143   hex5 = 7'b1111111;
144 end
145 endcase
146 end
147
148 // seven-segment display logic
149 always @(*) begin
150   case (pass1)
151     4'h0: z = 7'h3F;
152     4'h1: z = 7'h06;
153     4'h2: z = 7'h5B;
154     4'h3: z = 7'h4F;
155     4'h4: z = 7'h66;
156     4'h5: z = 7'h6D;
157     4'h6: z = 7'h7D;
158     4'h7: z = 7'h07;
159     4'h8: z = 7'h7F;
160     4'h9: z = 7'h67;
161     4'hA: z = 7'h77;
162     4'hB: z = 7'h7C;
163     4'hC: z = 7'h39;
164     4'hD: z = 7'h5E;
165     4'hE: z = 7'h79;
166     4'hF: z = 7'h71;
167     default: z = 7'h00;
168   endcase
169
170   case (pass2)
171     4'h0: zz = 7'h3F;
172     4'h1: zz = 7'h06;
173     4'h2: zz = 7'h5B;
174     4'h3: zz = 7'h4F;
175     4'h4: zz = 7'h66;
176     4'h5: zz = 7'h6D;
177     4'h6: zz = 7'h7D;
178     4'h7: zz = 7'h07;
179     4'h8: zz = 7'h7F;
180     4'h9: zz = 7'h67;
181     4'hA: zz = 7'h77;
182     4'hB: zz = 7'h7C;
183     4'hC: zz = 7'h39;
184     4'hD: zz = 7'h5E;
185     4'hE: zz = 7'h79;
186     4'hF: zz = 7'h71;
187     default: zz = 7'h00;
188   endcase
189 end
190
191 endmodule


```

5 Simulation Results

Displaying wrong password entered 123456 (-----) which is 0111111




Display |||| when correct password is entered 111746 which is 1111001

 


6 Experimental Results


Entering a wrong password

 

 
Displays Failed (----) and LED 5 stays off to show failed state (for extra credit)



Entering the correct password (111746)

 

Displays Unlock with (||||) also for extra credit added an LED5 to show it is unlocj

 

7 Summary

Our lab Project was to design a combinational digital lock that takes a password of 8bit of 3 pairs of numbers that displays on the DE1 SoC Board and tells user if the of its wrong by ----- and ||||| and LED ON if the correct password(11-17-46) is entered in this results are display on the board by the help of seven segment code. This experiment involved the design and implementation of a module lock using Verilog hardware description language. The module lock is a digital circuit designed to control access to a module or system by requiring the input of a specific password. The password is entered via two 4-bit inputs, and the lock transitions through different states based on the correctness of the password input. The design utilized D flip-flops for state storage and combinational logic for password verification and output generation.

8 Lessons Learned

I had problems with this project a lot like I had a hard time storing 3 pairs of numbers I could do one and it will display if wrong or not then decided to use register to store values later couldn't put it together, I knew it could work but decided finally to take the

state transition approach. I also learned the significance of proper state machine design and combinational logic in implementing access control mechanisms. Understanding how to define states, transitions, and outputs in Verilog code allows for the creation of complex digital systems with specific functionalities.

END OF DOCUMENT